

Solid-State Oscilloscope


Circuit details of a test instrument designed for work on colour TV receivers.

by Michael Phillips

To be capable of performing all the measurements needed on a colour television receiver an oscilloscope must be able to provide accurate results from d.c. up to the sub-carrier frequency of about 4.4 MHz. Experiments with a colour decoder confirmed that an elderly, low-frequency oscilloscope did not have sufficient bandwidth for such work and it was decided that the cheapest way of obtaining improved performance was to construct a new vertical amplifier as an add-on unit using the existing tube and e.h.t. supply. This was later extended to include a new timebase, X amplifier and square-wave calibrator.

An important requirement of this type of conversion is that the amplifiers should be designed to supply the high deflection voltages, 250 to 300 V peak-to-peak, needed by older types of oscilloscope tube. This was made easy by the availability of inexpensive silicon transistors intended for use as video amplifiers in television receivers, resulting in simple, low-power circuits giving high output voltages at bandwidths that would be difficult to achieve with valve amplifiers.

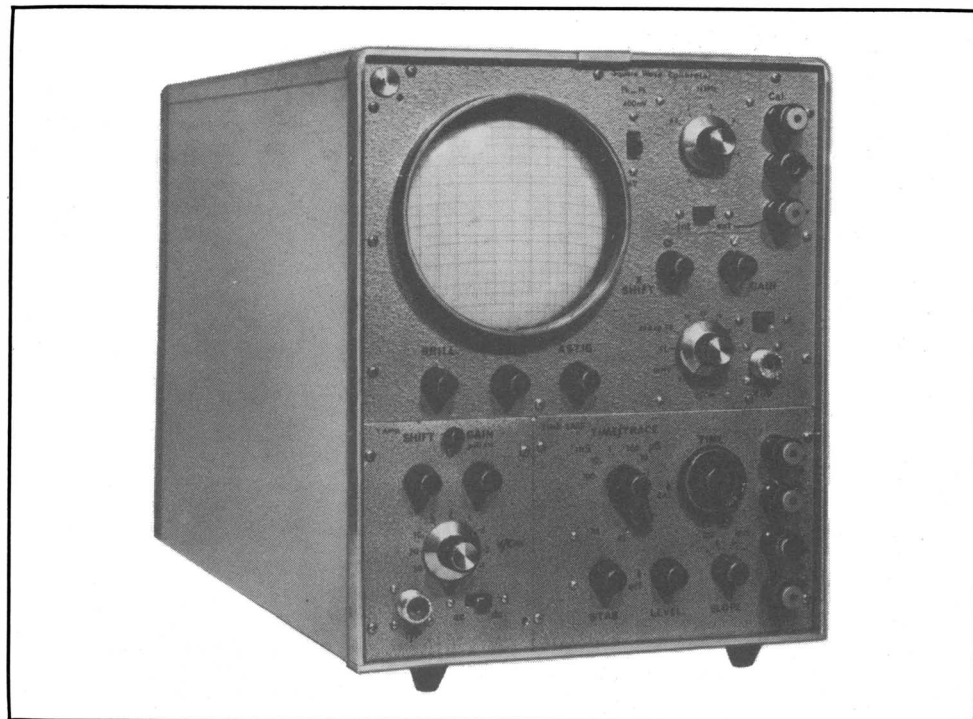Performance figures which follow refer to a 5CP1 tube with a supply of 1.25 kV plus an additional 1.25 kV on the p.d.a. electrode and will be typical for most 13 cm. tubes of this vintage. With more modern, higher



sensitivity tubes these figures can be improved upon since both amplifier gain and output voltage swing requirements are less. Possible modifications to the circuits are described later.

Vertical amplifier

The response of the vertical amplifier is flat from d.c. to 6 MHz and is 3 dB down at 11 MHz, the maximum sensitivity being 100 mV per cm. The gain can be switched for a $\times 10$ increase with a reduction in the 3-dB bandwidth to 1.5 MHz. The circuit divides conveniently into two sections. Fig. 1 shows the pre-amplifier, which includes the input attenuator and all the controls, and Fig. 2 the output amplifier which should be situated as close to the tube base as possible. The input attenuator uses compensated potential divider sections presenting a constant input impedance of $1 M\Omega$ in parallel with approximately 20 pF. Attenuator switching sequences tend to be a matter of personal preference so a choice should be made from the values given in Table 1. For most purposes ordinary carbon resistors with a tolerance of 10% are

quite satisfactory and are much cheaper than high-stability types.

When using a high-impedance probe any difference in the input capacitance between different attenuator sections must be compensated for by adjustment of the probe trimmer. This can be avoided by connecting trimmer capacitors of about 10 pF maximum from each position of Sw_{2a} to earth. A suitable probe consists of a $9.1 M\Omega$ resistor shunted by a 3-12 pF trimmer and mounted in a metal tube (some cigar containers are ideal). The probe should connect to the oscilloscope through about



Table 1

Sensitivity	R_a (Ω)	R_b (Ω)	C_b (F)
200 mV	510 k	510 k	20 p
300 mV	680 k	390 k	39 p
500 mV	820 k	200 k	68 p
1 V	1 M	110 k	180 p
2 V	1 M	51 k	400 p
3 V	1 M	33 k	500 p
5 V	1 M	20 k	1 n
10 V	1 M	10 k	2 n
20 V	1 M	5.1 k	4 n
30 V	1 M	3.3 k	6 n
50 V	1 M	2 k	12 n

Values for the Y input attenuator of Fig. 1. A choice should be made for either 1-2-5 or 1-3-10 range sequences. C_a for each section is a 30 pF max. mica compression trimmer.

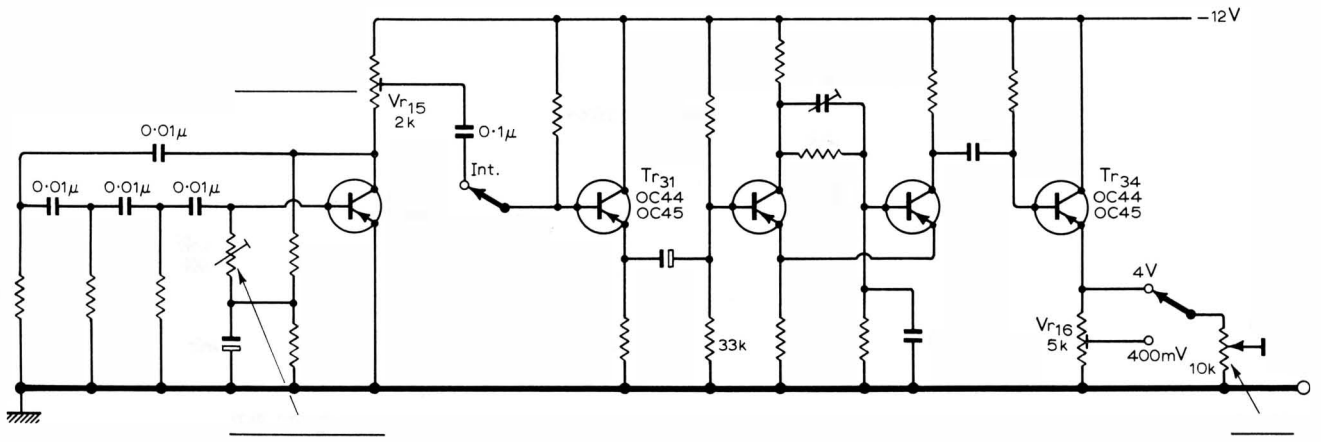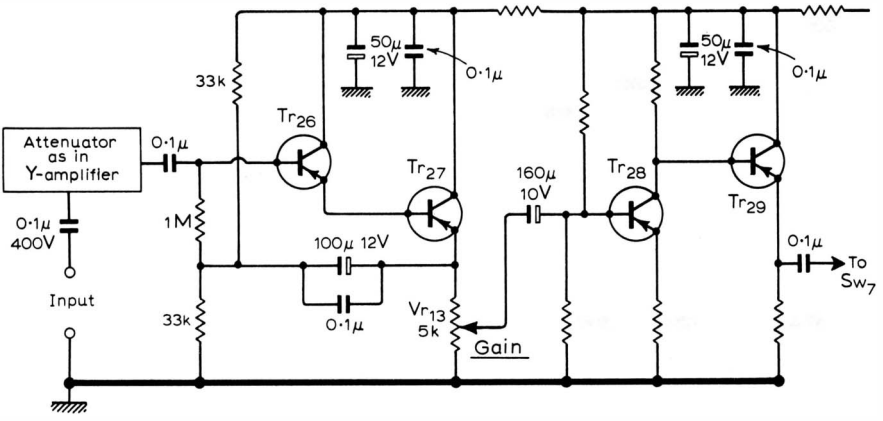Michael Phillips served in minesweepers during and after the war and then went to college in 1947. For five years, 1950-55, he was engaged on radio and test-gear development with Ultra Radio. He has been with Bush Radio, more recently Rank Bush Murphy, for the last 12 years and is now project leader for monochrome television development.





tor is similar to the one used in the Y pre-amplifier and is followed by the Darlington pair Tr_{26} and Tr_{27} , giving a stage gain of unity but an input impedance of several megohms. The amplifier which follows uses two transistors Tr_{28} and Tr_{29} as a common-emitter/emitter-follower pair. This last circuit, incidentally, is quite a useful one in its own right; it has a gain of ten and, with v.h.f. transistors such as those used in TV tuners and with a suitable peaking capacitor across the first emitter resistor, will maintain that gain to over 200 MHz.

For the X pre-amplifier most types of germanium h.f. transistors will be suitable or, with a reversal of all polarities, the silicon devices used in the other circuits.

Square-wave calibrator

This section generates a square wave with an output amplitude variable between 50 mV

and 4 V peak-to-peak from either an internal source at 10 kHz or at any frequency from 15 Hz to 20 kHz with a sine-wave input from an external a.f. generator. The circuit diagram in Fig. 6 shows a 10 kHz sine-wave oscillator Tr_{30} , an emitter-follower buffer stage Tr_{31} into which can also be switched the external input, and a Schmitt trigger circuit Tr_{32} and Tr_{33} to generate the square-wave. The emitter-follower output Tr_{34} feeds a simple attenuator which gives two ranges of output amplitude; 50 mV to 400 mV and 500 mV to 4 V. There are pre-set trimmers for adjusting the frequency and the mark/space ratio, and the trimmer capacitor in the Schmitt trigger circuit is used for setting an exact square-wave. Besides proving very useful for gain calibration, and adjusting the attenuator and probe compensation, the calibrator can also be used as a signal source for square-wave testing.

Power supplies

Supply for the 120–150 V h.t. line required by the output stages is most conveniently derived from a higher voltage by means of a cathode-follower valve as shown in Fig. 7. This provides an easily adjustable, low impedance source and the current, about 58 mA, is within the ratings of a small power valve such as the EL84. Four low voltages required can be obtained from a small transformer and rectifiers via transistors, Tr_{35} to Tr_{38} , connected as emitter-followers. Power dissipated in the transistors is about 110 mW, except for Tr_{38} where it is about 900 mW, and in this position it is suggested that an AC127 or similar is used. If small power transistors like the OC81 are used for Tr_{35} and Tr_{38} there will be surplus power available for connecting to external units such as a wobulator. A BC107 is suitable for Tr_{37} and it can be mounted with the time-base assembly. The three other power supply transistors should be clipped to an aluminium plate or chassis to provide a heat sink.

Modifications

As explained at the beginning of this article the performance figures quoted throughout refer to the use of a 5CP1 tube under specified working conditions which give a deflection sensitivity of about 20 V/cm. If a more modern tube with better sensitivity is used, then high drive voltages will not be needed and the collector supply voltage to the output stages can be reduced to some 60 to 80 V. If the same basic input sensitivities of 100 mV/cm and 10 mV/cm are to be retained, then the overall gain must be reduced by increasing the values of the feedback resistors linking the bottom emitters of the long-tail pairs. Changes will also be needed to the values of the various frequency-compensating capacitors. The resulting increase in bandwidth will be most noticeable in the $\times 10$ gain position and, as an estimate, the 10 mV bandwidth with a DN17-78 tube (7.6 V/cm) should be about 4.5 MHz at -3 dB.

There are, of course, many other facilities that can be included to make a more complete oscilloscope system and it is the purpose here to suggest a few so that switching or the necessary space can be allowed for in case such circuits are required later. If the leading edge of a pulse is used to initiate the timebase sweep then this section of the input signal will not be visible for study unless a time delay is incorporated in the path of the vertical output amplifier. Such a delay can be introduced by using a properly terminated delay line of about 400 ns, and of adequate bandwidth, between the cathode of V_1 and the base of Tr_2 . It should be switched out of circuit on the $\times 10$ gain range where the degraded rise-time does not warrant its use. The time-base trigger circuit must, of course, be fed from the cathode of V_1 and an additional trigger amplifier will be required.

For examining television waveforms, a delayed time-base sweep is needed. This can be achieved by duplicating the time-

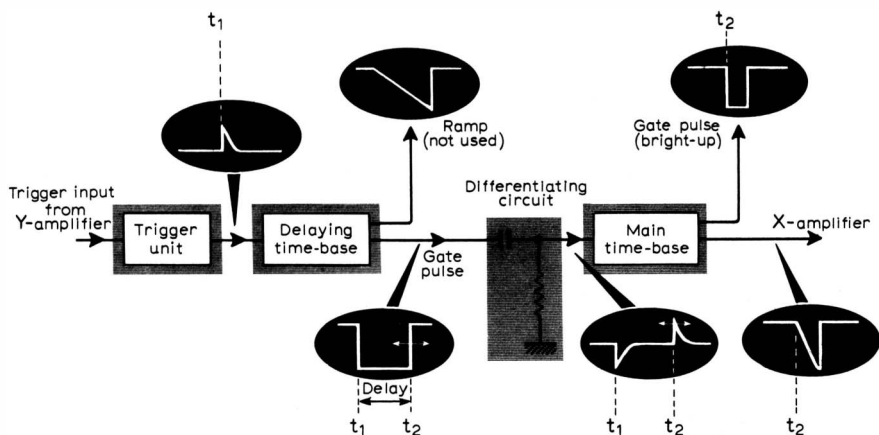


Fig. 8. Diagram showing use of additional time-base circuit to give delayed sweep for examining television video waveforms. Both time-bases are triggered by positive-going pulses only.



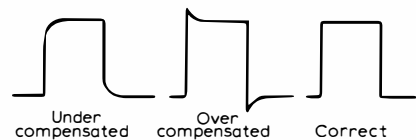


Fig. 9. Effect produced on square-wave by adjustment of compensating trimmers.

Fig. 10. General arrangement of units inside oscilloscope.

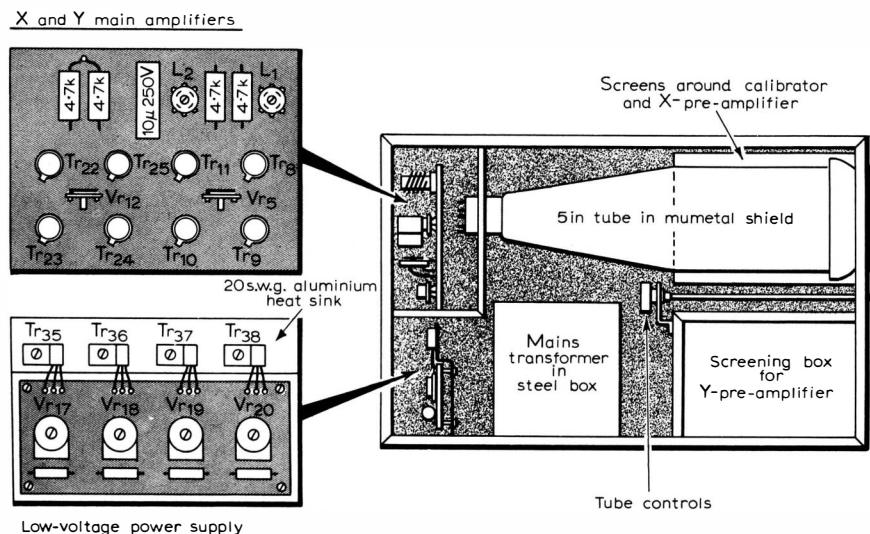

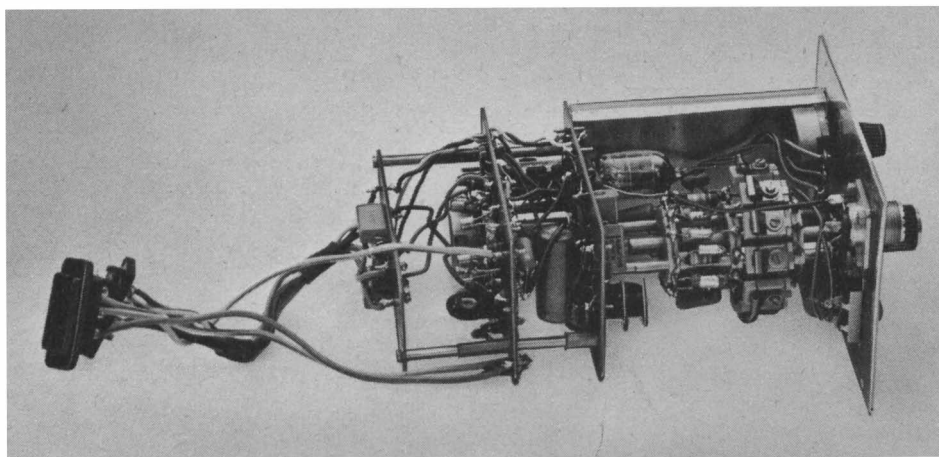

Photograph of the Y preamplifier module.

base circuit and driving it from the trigger unit. The differentiated gate pulse from the new unit is then used to trigger the main time-base. This description will probably be made clearer by referring to the block diagram in Fig. 8.

Setting-up and calibration

To set up the correct d.c. working conditions in the Y amplifier, first adjust for the following voltages: V_{r_1} to give 72 V at V_1 anode, V_{r_2} for 1V at Tr_3 base and V_{r_5} for 8.4 V at the base of Tr_6 ; all voltages positive with respect to the -12 V line. V_{r_2} is then finally re-adjusted for equal top and bottom limiting on a sine-wave signal of sufficient amplitude to cause overloading. During all these adjustments the Y shift control should be set for zero volts between the bases of Tr_2 and Tr_5 . Since the amplifier is directly coupled, the preset gain controls V_{r_3} and V_{r_4} can be adjusted using a d.c. supply and a voltmeter as the calibration source.

Without access to a good oscilloscope the problem of adjusting the various frequency-compensating trimmers is rather like that of the chicken and the egg. Fortunately however, we can set as a starting point the $\times 1$ gain 100 mV position on the attenuator. In the absence of any instability the response of the amplifier should be as specified with no irregularities and, since there is no input compensation, this position can be used for displaying the calibrator unit output. $V_{r_{16}}$ should be set for unity mark/space ratio and the trimmer in the Schmitt trigger C_d , to give a flat-topped square-wave. The effect on the waveform due to the adjustment of this and the other compensating trimmers is shown in Fig. 9. Once the output from the calibrator unit is satisfactory it can be used for setting the attenuator trimmers (C_a in Fig. 1), by adjusting each one in turn to give a flat-topped square-wave display. The 50 Hz mains supply with a period of 20 ms forms a useful standard for setting the time-base range multiplier resistors, V_{r_9} to $V_{r_{11}}$, but for checking the shorter time decades and for setting the 1 μ s trimmer capacitor, a generator covering the appropriate frequencies will be needed.

Construction

Since tube sizes and the type and volume of e.h.t. supplies can vary a great deal it is not the intention here to describe the construction in detail. In the title photograph is shown the oscilloscope which has evolved from a series of re-builds as circuit improvements were made, from the original add-on units mentioned in the introduction. It comprises basically a box frame-work made of 1.25 cm angle aluminium. The various circuit sections are built as separate units on s.r.b.p. perforated panels (plain Veroboard) with plug and socket connections to the power supplies. The general disposition of the units is shown in Fig. 10.

The Y preamplifier and the trigger/time-base unit plug-in to the front of the instrument. Construction of the pre-amplifier is illustrated in the photograph above. The attenuator switch uses three wafers, the resistors R_a and the trimmers C_a being connected in parallel between the front two wafers, while R_b and C_b connect to the last wafer which is used solely as a common earth. The first panel is used for mounting V_1 , Tr_1 and their associated components, the remainder of the amplifier is wired on the second panel and the supply decoupling components on the rear one. The time-base is quite straightforward except for the choice of a time switch. The alternatives are: an eighteen way switch, separate six and three way switches or, the solution used here, two switches with concentric spindles.

Since the only real sources of heat are the tube and the two valves there are no ventilation problems, two 25 mm holes in the bottom and expanded metal mesh over half the back being all that is necessary.

REFERENCES

1. 'A Wideband Oscilloscope Probe', by L. Nelson-Jones. *Wireless World* August 1968, page 275.
2. Wescon/66 Technical Papers. Part 6. Session 11 on Field Effect Transistors.
3. 'Emitter-Timed Monostable Circuit', by B. Gilbert. *Mullard Technical Communications*, July 1961, P. 345.
4. 'Oscilloscope Timebase Generator', by B. Gilbert. *Mullard Technical Communications*, March 1964, p. 276.

The series of articles on the *Wireless World* Oscilloscope which appeared during 1963 and 1964, and which is now available in a set of five booklets, will be found generally useful for references.

Corrections

Some other Measuring Rectifiers

Owing possibly to some clod of earth still adhering to me after resurrection, or to a misguided attempt to be concise, an erroneous statement (in italics, too!) got through in "Some other Measuring Rectifiers" (Feb. issue). While it is true that the bridge rectifier type of voltmeter would correctly read r.m.s. values of square waves if it were calibrated in its natural mean values (because the mean and r.m.s.—and peak—values of square waves are all the same) it would *not* do so if the calibration incorporated the 1.11 factor converting sine-wave mean to r.m.s. My apologies.—"CATHODE RAY"

High Impedance Multimeter

The author, V. R. Krause, regrets an error that occurred in Fig. 3 of his article "High Impedance Multimeter" in the February issue. The labelling of the range switch, S_{2a} , is reversed; the 1V range switch position should be labelled 300V.

Circuit Ideas

In Fig. 2 in the contribution "A unity gain amplifier for very low-frequency filters" on p.15 in the January issue the base of the output transistor should be connected to the collector of the preceding p-n-p transistor; *not* to the junction of the complementary emitters as shown.