

# Electronic thermometer

Simple sensing diode provides accurate and reliable temperature measurement

by A. S. Henderson

Although several designs for electronic thermometers have been published, most of these have either been complicated or low performance devices. This design has been kept simple for reliable operation, and offers an accuracy within 1% of f.s.d.

The most important part of an electronic thermometer is the sensing device which, in most cases, should be small, have a low thermal capacity, generate a large signal, respond linearly to temperature variations, abstract or dissipate very little energy and have a long life. Several devices such as thermistors, transistors and special i.c.s were considered, but the most attractive device appeared to be a miniature signal diode. It is generally accepted that, with a constant current, the forward voltage across a silicon diode reduces by 2mV per degree increase in junction temperature.

This can be expressed as

$$\Delta V = \frac{kT}{q} \ln V_f$$

where  $k$  is Boltzmann's constant and  $q$  is the charge on the electron. As  $k$  and  $q$  are fixed, the change in voltage must be linearly connected to temperature, and the physical constants of silicon give 2mV/°C.

To test this parameter, six batches of 100 miniature signal diodes were evaluated as shown in Fig. 1, using a 9 to 15V d.c supply connected in series with a 10k $\Omega$  resistor, a multimeter and a diode. The diode under test was cycled from 0°C to 100°C with a forward current of exactly

1mA at 0°C. As there was no detectable change in forward current, this was assumed to be constant. The forward voltage drop,  $V_f$ , of each diode was measured at ambient temperature to record the spread in  $V_f$  within a batch. These values were grouped in 5mV steps, and the distribution of  $V_f$  within six batches of 100 silicon devices is shown in Fig. 2.

From each type, two devices from the outer distribution spread, ignoring the odd wild values, and three from the central concentration were assembled into probes and tested for  $V_f$  at 0°C and 100°C. The correlation between  $V_f$  at 0°C and the voltage excursion,  $\Delta V$ , over 100°C for four types is shown in Fig. 3. The 1N3063, 1S44 and 1N4154 showed no apparent correlation and have been omitted.

A batch of germanium diodes, type 1N3470, was also tested and Fig. 4 shows the distribution of  $V_f(\text{amb})$  for these devices. An ideal device, indicated in Fig. 3 by a dotted line marked 2mV/°C, has a

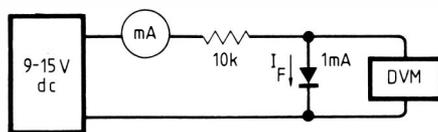


Fig. 1. Test circuit to measure  $V_f$ .

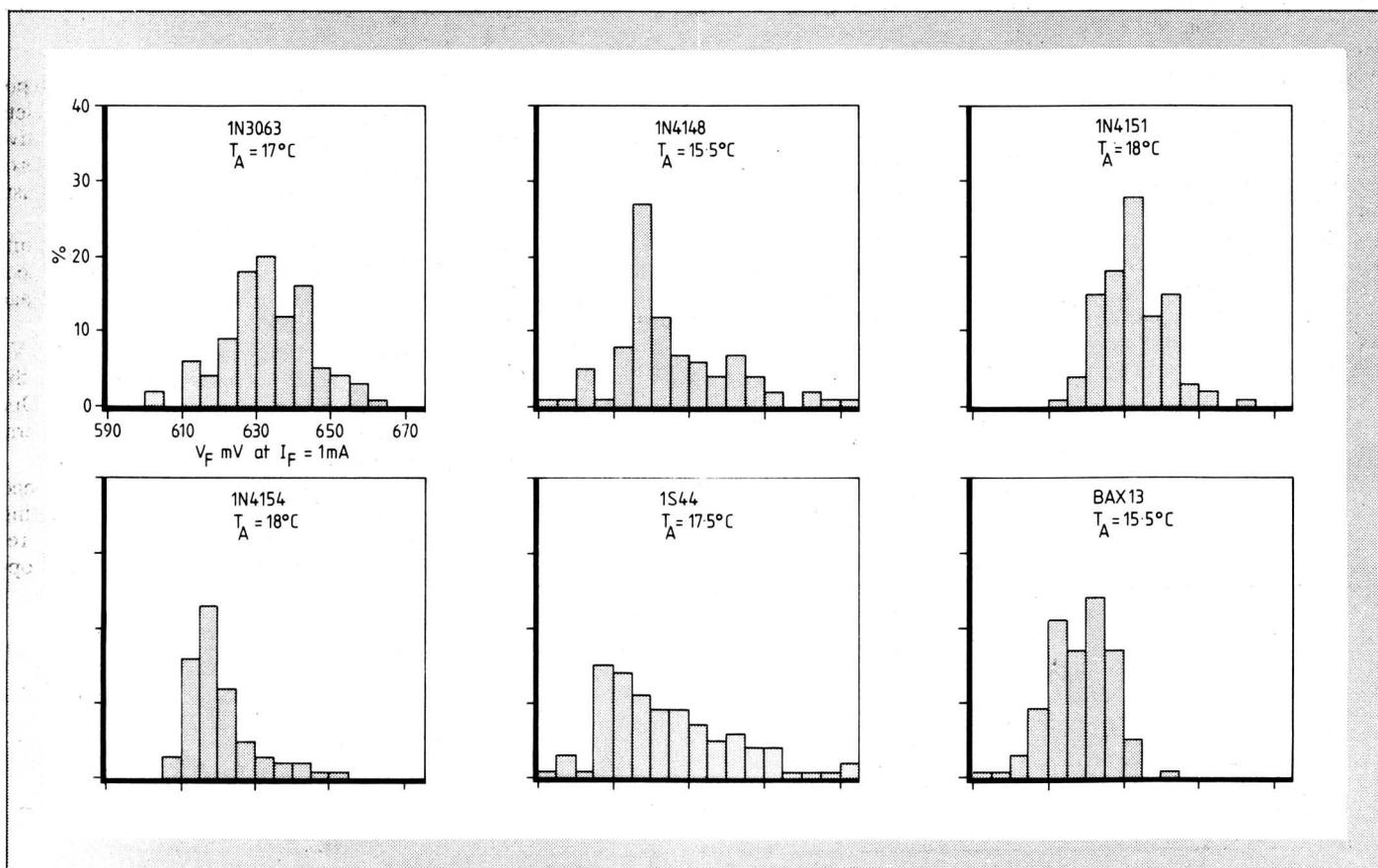


Fig. 2. Distribution of  $V_f(\text{amb})$  for six types of silicon diode.



amp in Fig. 7 and use it as a comparator. However, because the change in temperature is proportional to temperature difference, the probe will not quite reach the ambient temperature and over the last fraction of a degree the output changes very slowly. This will cause the op-amp to oscillate for several seconds before switching and may permit switching by thermal noise. Introducing hysteresis by positive feedback is an effective way to stop the oscillation, but this produces an unacceptable dead band. The problem can be overcome by using a dual op-amp with one half connected as in the original circuit and the output signal fed to the second half connected as a comparator with positive feedback. As the output signal is more than five times greater than the input, the dead band is reduced to less than 0.5°C. The combined indicator and comparator circuit is shown in Fig. 9. In the prototype some 741 op-amps did not switch off the transistor. If this occurs, a signal diode should be connected in series with the emitter to raise the base voltage.

Because this is a low-gain, low-impedance circuit, construction is not critical and earthing the 0V line enables a cheap and simple probe to be assembled as shown in Fig. 10. To prevent mains hum a screened lead should be used with the probe.

### Multi-channel operation

As explained earlier, diodes of the same type do not exhibit exactly similar characteristics so multi-channel operation is not

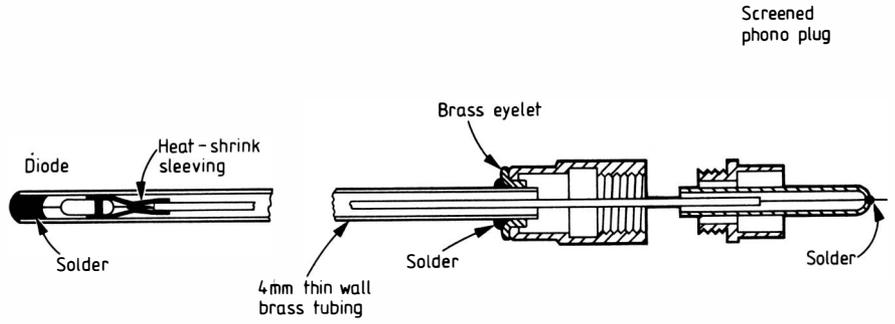


Fig. 10. Temperature probe assembly.

straightforward. Using several meters or cermet potentiometers is expensive, and wire-wound types suffer from poor resolution. Matching the diodes provides a low-cost solution and the test circuit in Fig. 11 enables the devices to be sorted into 0.5mV or 0.25°C groups very quickly. The test circuit does not measure  $V_F$  directly but the differences in  $V_F$  compared with a preset value, which permits the use of the most sensitive voltage range.

When switching two or more probes at the input to the indicator circuit, the switch must be a make-before-break type so that the op-amp input is always connected. For special applications it is easy to modify the circuit. Closely matched op-

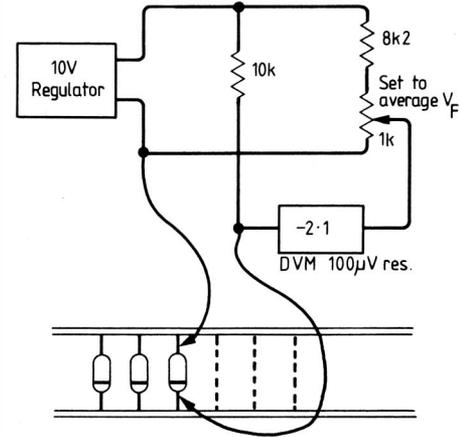


Fig. 11. Test circuit for matching sensing diodes.

amps as in the 747 minimise temperature drift even in a high-sensitivity differential circuit.

### Calibration

Calibration is simple and only requires distilled water. Prepare a tray of ice cubes from the distilled water, half fill a suitable container with the ice cubes and add the same amount of cold tap water. Stir thoroughly until the ice cubes are about half their original size, insert the probe and, when the meter reading stabilizes, adjust the 0°C control so that the meter reads zero. The mixture should be stirred again and the adjustment checked. Next, boil some distilled water, insert the probe and repeat the procedure for the 100°C control.

For intermediate scale lengths such as 0 to 40°C, proceed as above with a voltmeter connected between the cal point and 0V. Note the voltages at 0°C and 100°C, the output voltages at intermediate temperatures will be exactly proportional. Although diodes do not have the same temperature coefficient of forward voltage, the voltage changes linearly with temperature. When calibrating an intermediate scale always start at the bottom end with water about 5°C hotter than the minimum value. Insert the probe and calculate from the calibration cycle the output voltage at the minimum value. When the voltmeter agrees with the calculated value, adjust the 0°C control for zero. Repeat for the maximum value and adjust the 100°C control for full scale. It is better to use the cooling cycle rather than the heating cycle because cooling takes place more smoothly and uniformly. □

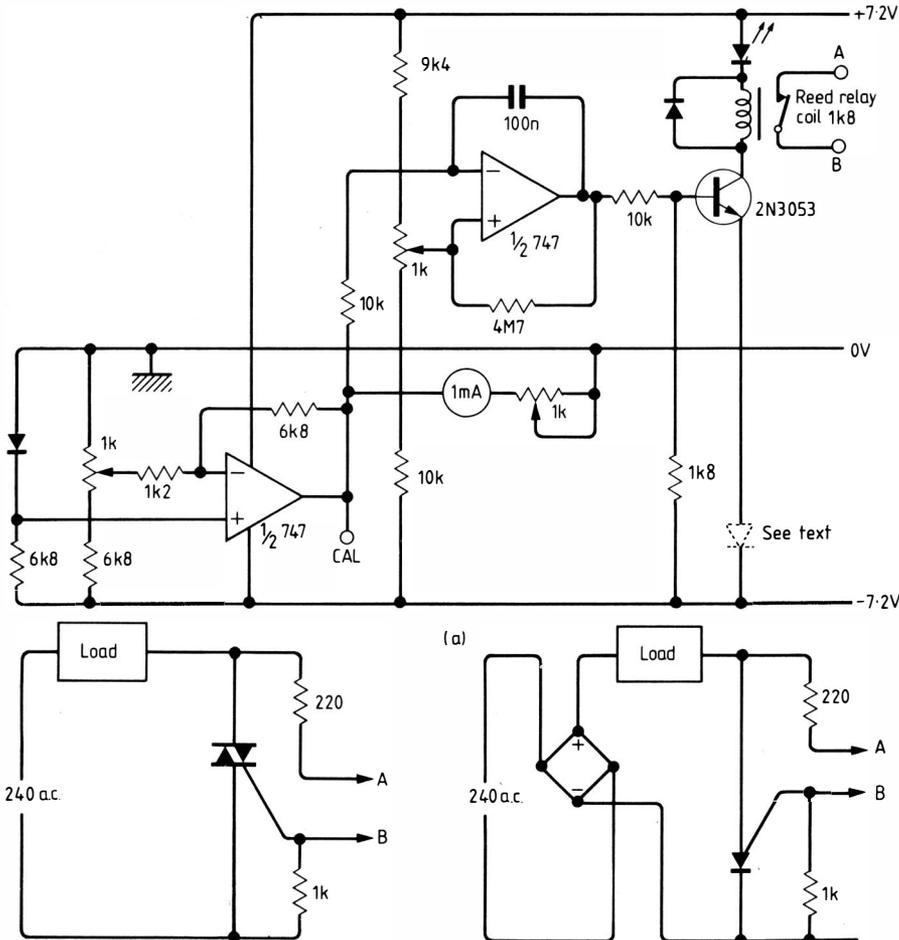


Fig. 9. Temperature indicator and comparator switch. The relay contacts can switch a small load or trigger the optional triac/s.c.r. circuits.